

## 8.27 - Notes

### ELE239

#### AND Truth Table

A	B	Y
1	1	1
1	0	0
0	1	0
0	0	0

#### NAND Truth Table

A	B	Y
1	1	0
1	0	1
0	1	1
0	0	1

#### OR Truth Table


A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0


#### NOR Truth Table

A	B	Y
1	1	0
1	0	0
0	1	0
0	0	1


## Basic Ladder Logic - IEC Symbols

### Inputs:

NO - 

NC - 

### Outputs:

Coil - 

Negated Coil - 