

## 9.04 - Notes

### ETR113

Voltage: Potential difference in charge between two points

Current: Rate of flow of electrons in a single instance

Resistance: Material resistance to current


Ohm's Law: The relationship between these elements

Volts = V

Ampers (Amps) = I

Resistance (Ohms) =  $\Omega$

$$V = I \cdot R$$

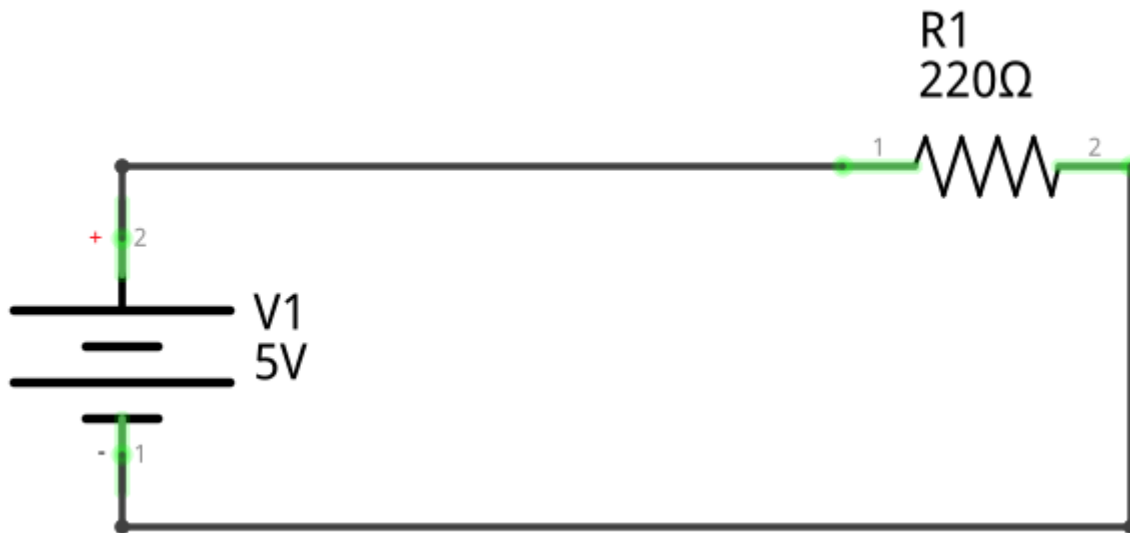

Solve for I:

$$V = I \cdot R$$

$$5 = I \cdot 220$$


$$\frac{V}{R} = I$$

$$\frac{5}{220} = ?$$


$$I = .0227 A$$

$$I = 22.7 mA$$

## Series Circuit: Voltage Divider

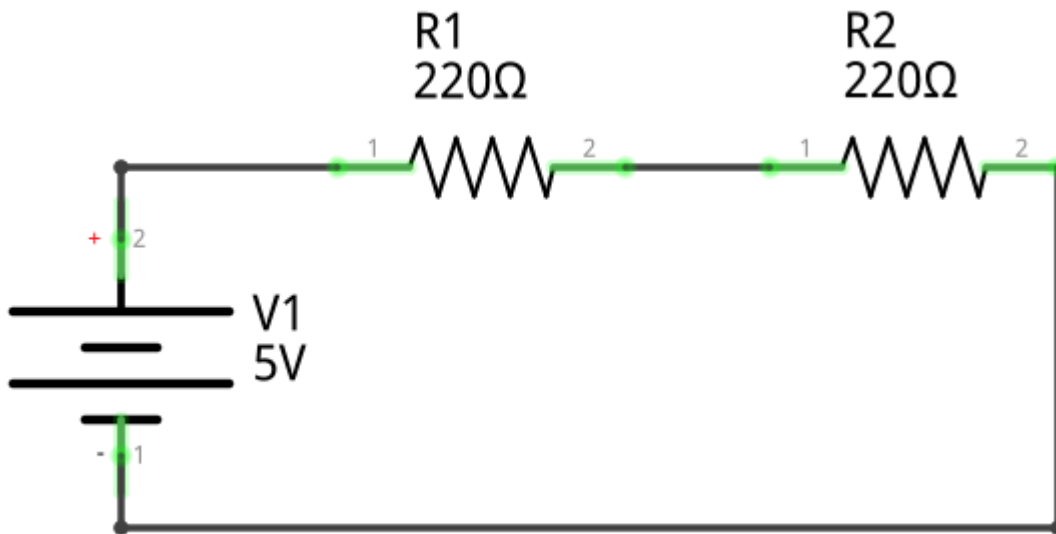

## Parallel Circuit: Current Divider

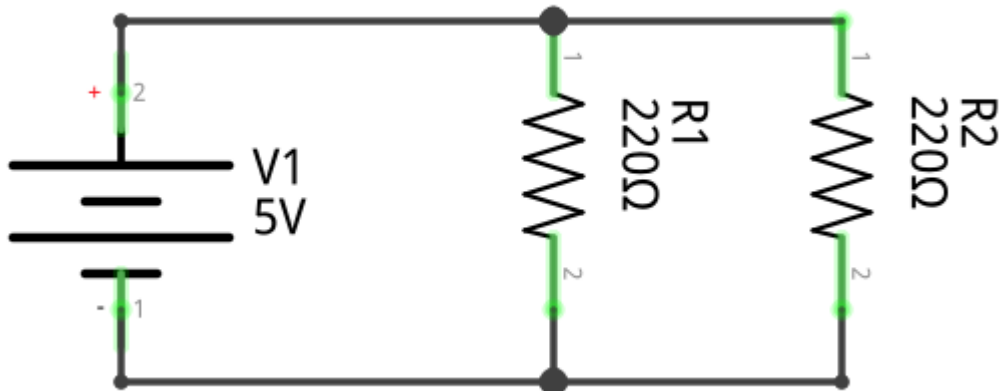

## Properties of Series Circuits:

Total Resistance = All resistances added together

$$R_T = R_1 + R_2$$

Resistor Value of LED: Find values on datasheet

$$\frac{(V_S - V_F)}{I_F}$$